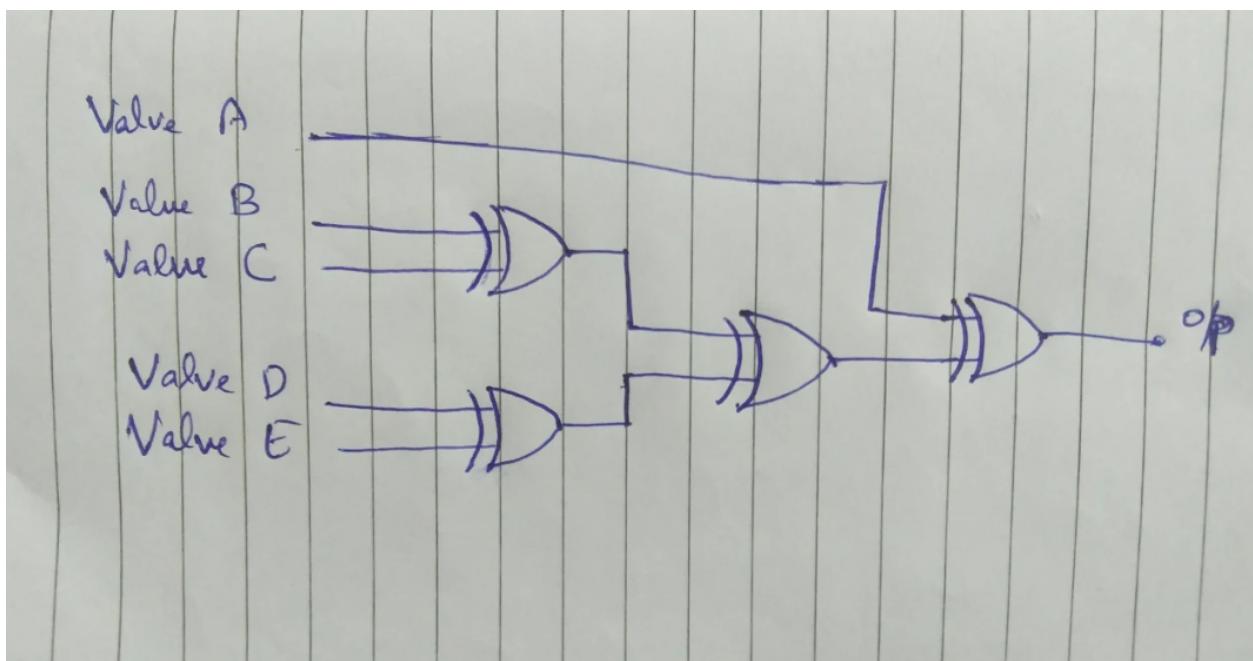


## LEVEL-4 ANSWER KEY

ANSWER: 1



ANSWER: 2

Ans). The question had mentioned of Mod 2 & Mod 5 counter, so the contestants could have used a single IC 7490 to get the required pattern or even using Mod 2 & Mod 5 separately is also good.

Q. The number sequence to be generated is :


A → E → C → G → J → B → F → D → H → J

0 → 4 → 2 → 6 → 8 → 1 → 5 → 3 → 7 → 9



To get this pattern, give the main clock to Mod 5's clk, connect the MSB of Mod 5 say  $Q_0$  to the ifp clock of Mod 2 counter. In doing so, you will generate the pattern as 0 → 2 → 4 → 6 → 8 → 1 → 3 → 5 → 7 → 9.

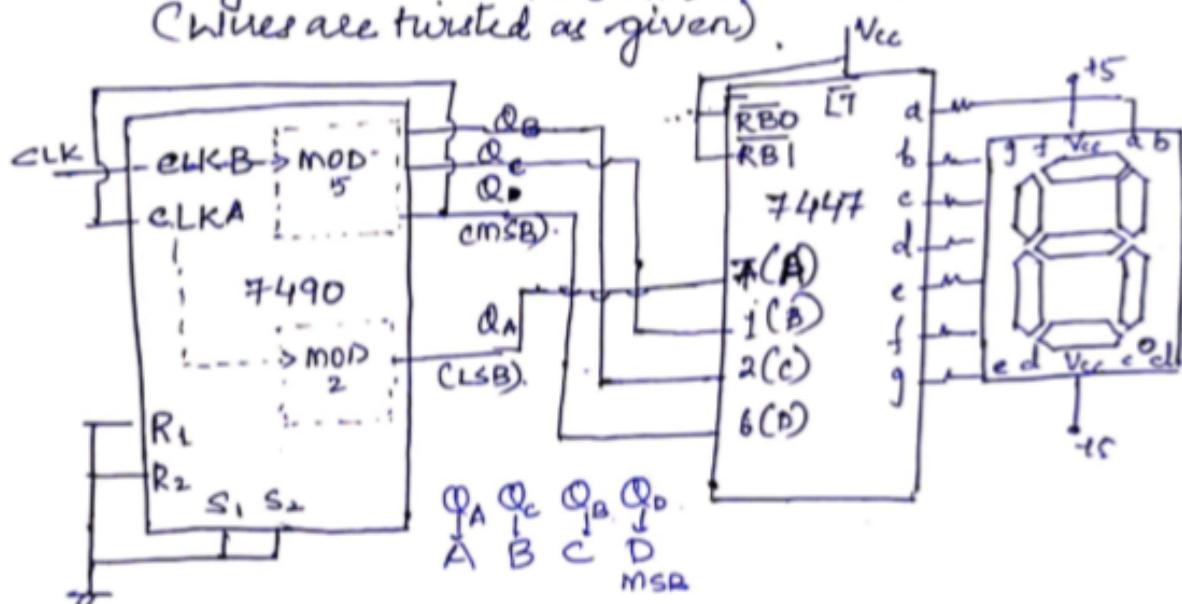But to get the required pattern, here is the twist. The ifp of 7 segment display driver should be given as  $Q_D Q_B Q_c Q_A$ , where  $Q_D$  is the MSB. (Wires are twisted as given).



## ANSWER: 3

To produce a sine wave at the output, the control signals driving the mosfet drivers(IR2101) must be changed. Currently it is running in fixed PWM mode.(Triangle with a single reference from potentiometer). 50% duty cycle

Change the control signal by applying a 50Hz sine wave A = 5Vpp < 8Vpp(TRI-wave) with offset = 4V(Triangle has an offset of 4V) to the comparators,Instead of the POT.



Also the triangle wave frequency must be increased from 50Hz to 5 – 10KHz.

### Modified Circuit.

Sine wave ,F = 50Hz,A = 5Vpp

Triangle wave F = 5-10KHz,A = 8Vpp

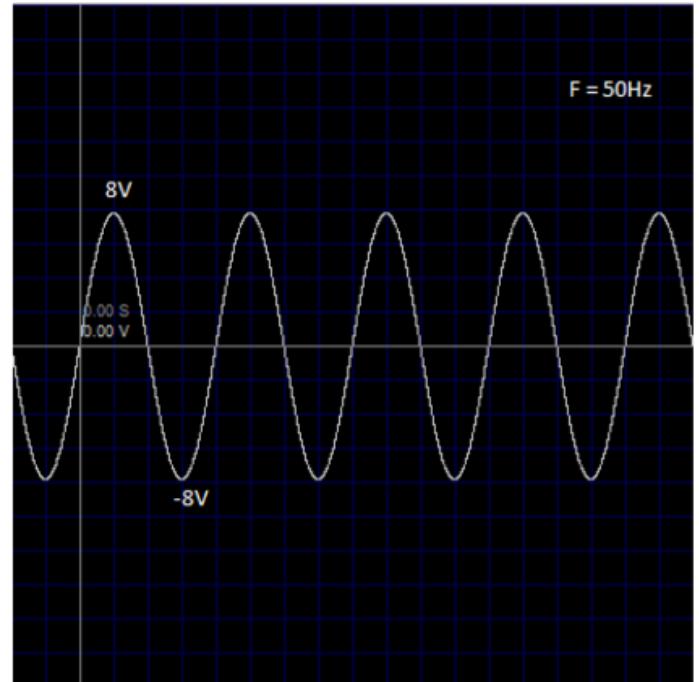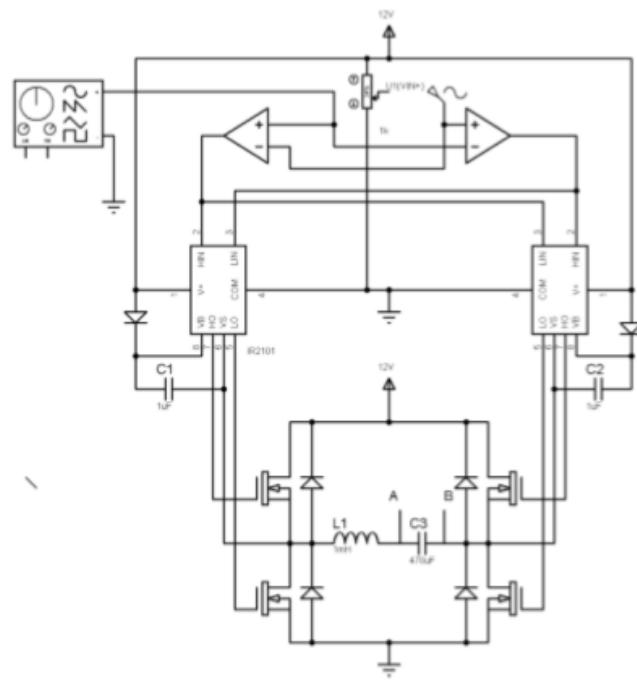Add a LC low pass filter at the load to get sine wave at the output.










LC low pass with cut off < 1Khz

Add sine wave f = 50Hz,offset = 4V

Increase triangle wave freq 5-10Khz

Add lc low pass filter.

## ANSWER: 4

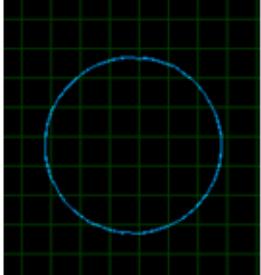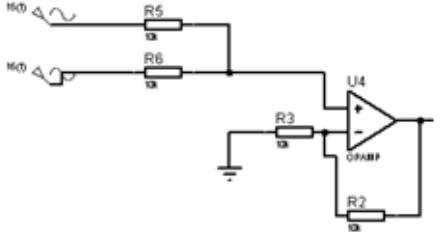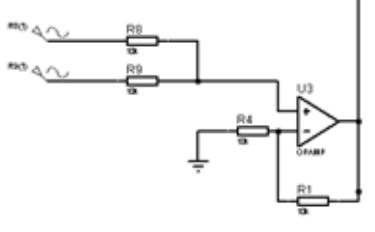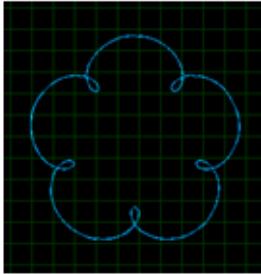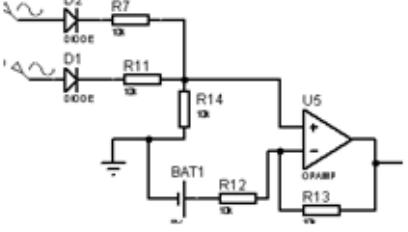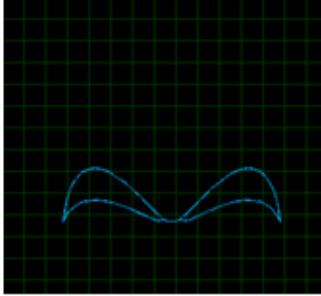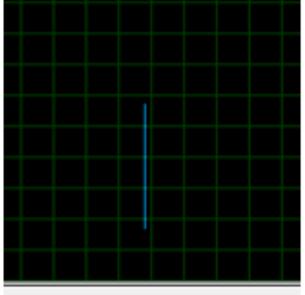X	Y	Transfer Chara
3V 400Hz Sin Phase Shift=0	3V 400Hz Sin Phase Shift=270	
Wave 1:4V 400Hz Sin, Phase Shift=0 Wave 2:1V 2.4Khz Sin, Phase Shift=180 	Wave 1:4V 400Hz Sin, Phase shift=270 Wave 2:1V 2.4Khz Sin, Phase Shift=90 	
5V 400Hz Sin, Phase Shift=0	Wave 1:1.5V 800Hz Sin, Phase shift=180 Wave 2:3V 800Hz Sin, Phase shift=0 	
Ground	2V 800Hz Sin, Phase shift=0	

The above wave forms are generated and multiplexed using 4051 mux at 200Hz

